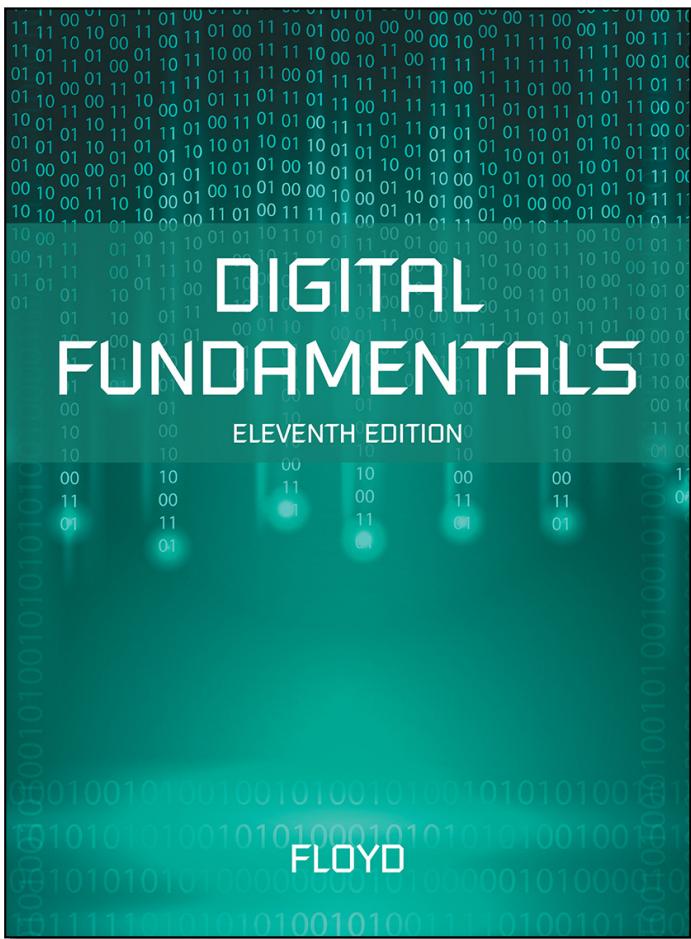


# Digital Fundamentals

ELEVENTH EDITION



## CHAPTER 4

Boolean Algebra  
and Logic  
Simplification

# Adição Booleana

- A adição booleana é equivalente à operação OR
- As regras básicas são ilustradas com sua relação com a porta OR

$$0 + 0 = 0$$

A logic diagram showing a single OR gate. It has two inputs, both labeled '0', and one output. The output is labeled '0'. The gate is shaded light blue.

$$0 + 1 = 1$$

A logic diagram showing a single OR gate. It has two inputs, the left one labeled '0' and the right one labeled '1', and one output. The output is labeled '1'. The gate is shaded light green.

$$1 + 0 = 1$$

A logic diagram showing a single OR gate. It has two inputs, the left one labeled '1' and the right one labeled '0', and one output. The output is labeled '1'. The gate is shaded light orange.

$$1 + 1 = 1$$

A logic diagram showing a single OR gate. It has two inputs, both labeled '1', and one output. The output is labeled '1'. The gate is shaded light green.

# Multiplicação Booleana

- A multiplicação booleana é equivalente à operação AND
- As regras básicas são ilustradas com sua relação com a porta AND

$$0 \cdot 0 = 0$$

A logic gate symbol representing an AND gate. It has two input lines entering from the top, both labeled with the value 0. One output line exits from the bottom, also labeled with the value 0.

$$0 \cdot 1 = 0$$

A logic gate symbol representing an AND gate. It has two input lines entering from the top, the left one labeled 0 and the right one labeled 1. One output line exits from the bottom, labeled 0.

$$1 \cdot 0 = 0$$

A logic gate symbol representing an AND gate. It has two input lines entering from the top, the left one labeled 1 and the right one labeled 0. One output line exits from the bottom, labeled 0.


$$1 \cdot 1 = 1$$

A logic gate symbol representing an AND gate. It has two input lines entering from the top, both labeled 1. One output line exits from the bottom, labeled 1.

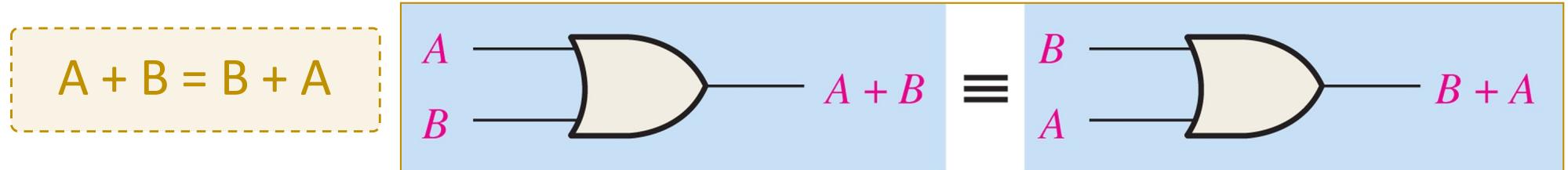
## PROPRIEDADE COMUTATIVA

As **propriedades comutativas** são aplicadas à **adição** e **multiplicação**.

- ✓ Para adição, a propriedade comutativa afirma que a ordem em que as variáveis são combinadas com **OR não fazem diferença**.



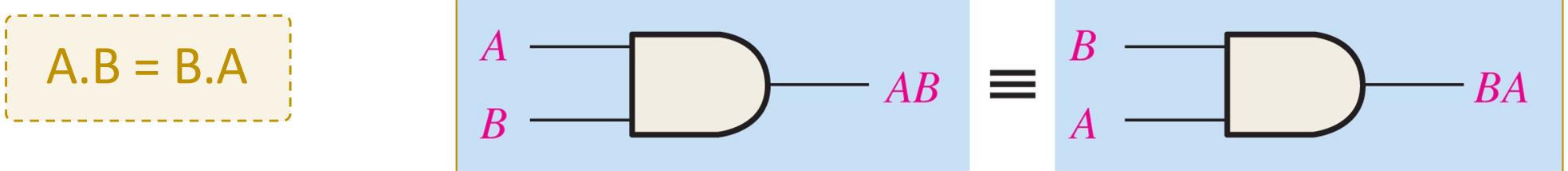
- ✓ Para multiplicação, a propriedade comutativa afirma que a ordem em que as variáveis são colocadas em **AND** também **não fazem diferença**.



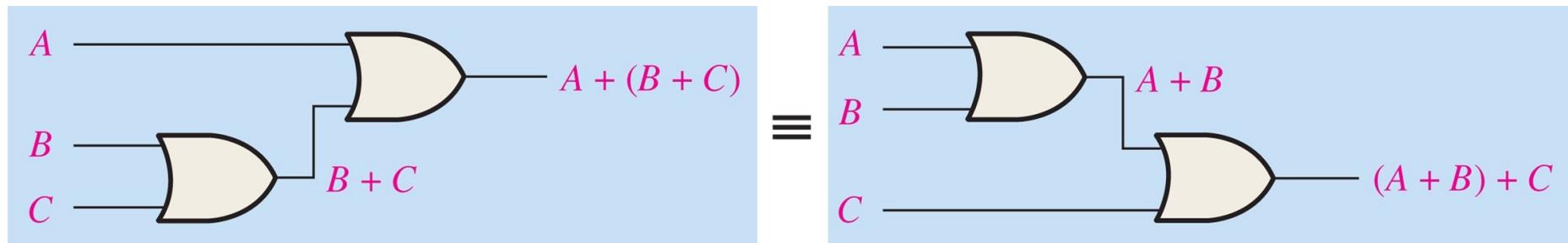
## PROPRIEDADE ASSOCIATIVA

As **propriedades associativas** são aplicadas à adição e multiplicação.

- ✓ Na adição, ao usarmos um **OR** em mais de duas variáveis, o resultado é o mesmo, **independentemente do agrupamento das variáveis**.



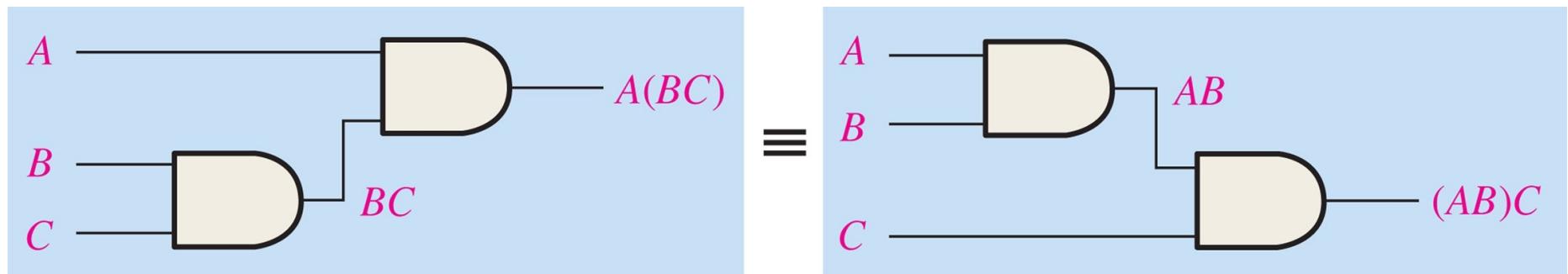- ✓ Na multiplicação, ao usarmos uma **AND** em mais de duas variáveis, o resultado é o mesmo, **independentemente do agrupamento das variáveis**.




## PROPRIADE DISTRIBUTIVA


A **propriedade distributiva** é uma **propriedade de fatoramento**. Isto é, uma variável comum pode ser fatorada de uma expressão, assim como encontramos na álgebra.

$$\mathbf{AB + AC = A.(B+C)}$$

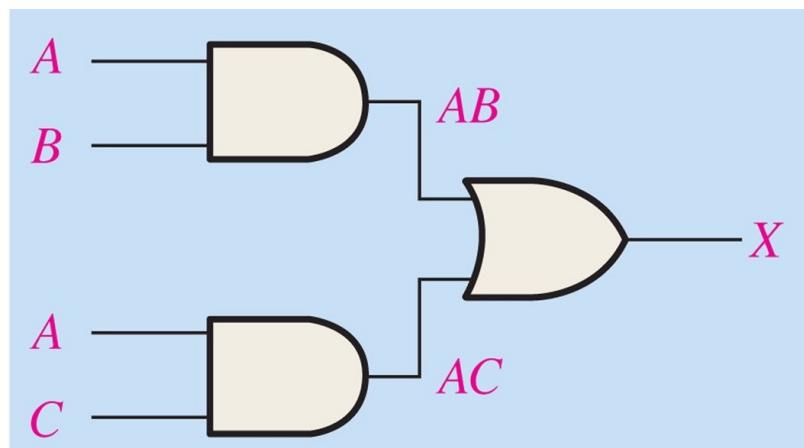- ✓ A propriedade distributiva pode ser ilustrada com circuitos equivalentes:



$$X = AB + AC$$

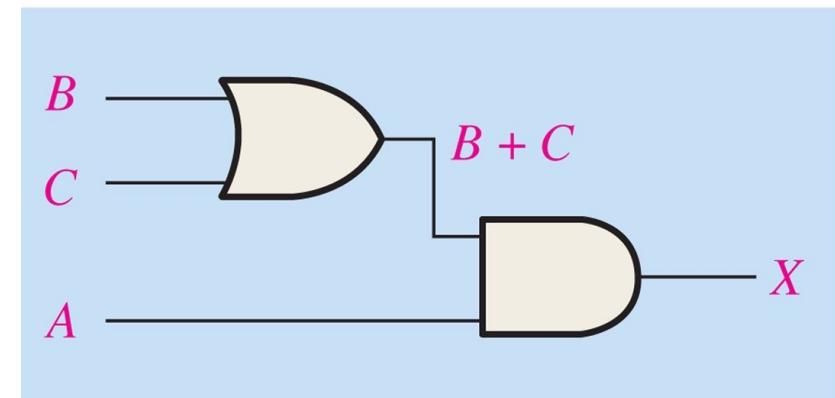

$$X = A(B + C)$$

**A**, **B**, ou **C** podem representar uma única variável ou uma combinação de variáveis

## TABLE 4-1

Basic rules of Boolean algebra.

---

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

$$10. A + AB = A$$

$$11. A + \bar{A}B = A + B$$



$$12. (A + B)(A + C) = A + BC$$

---

# Rules of Boolean Algebra (1-2)

1.  $A + 0 = A$
2.  $A + 1 = 1$
3.  $A \cdot 0 = 0$
4.  $A \cdot 1 = A$
5.  $A + A = A$
6.  $A + \bar{A} = 1$

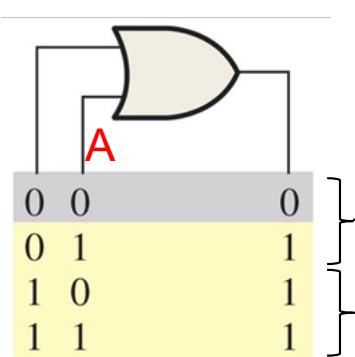
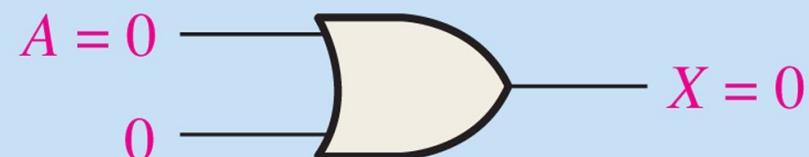
7.  $A \cdot A = A$
8.  $A \cdot \bar{A} = 0$
9.  $\bar{\bar{A}} = A$
10.  $A + AB = A$
11.  $A + \bar{A}B = A + B$
12.  $(A + B)(A + C) = A + BC$



$$X = A + 0 = A$$

OR

$$X = A + 1 = 1$$

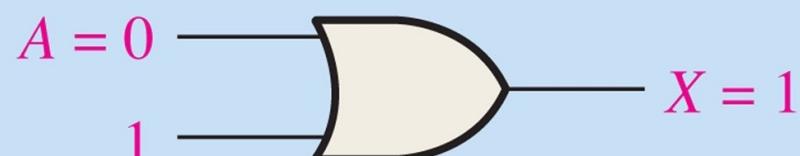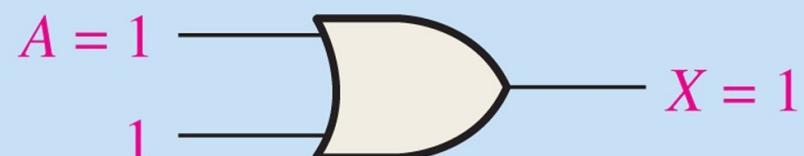

## Rules of Boolean Algebra (3-4)

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$7. A \cdot A = A$$


$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

$$10. A + AB = A$$

$$11. A + \bar{A}B = A + B$$

$$12. (A + B)(A + C) = A + BC$$

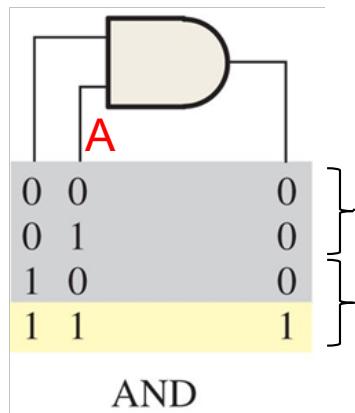



$$X = A \cdot 0 = 0$$

$$X = A \cdot 1 = A$$





## Rules of Boolean Algebra (5-6)

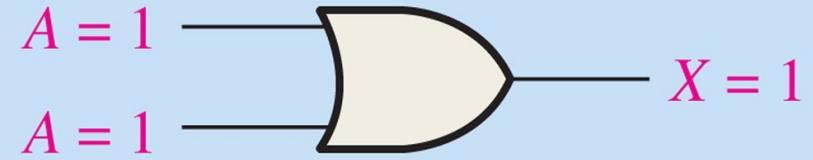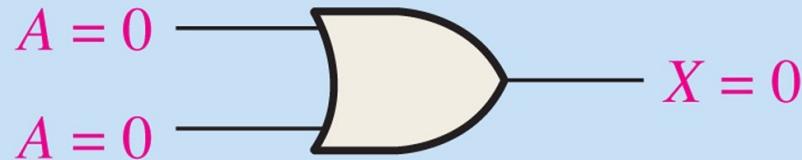1.  $A + 0 = A$
2.  $A + 1 = 1$
3.  $A \cdot 0 = 0$
4.  $A \cdot 1 = A$
5.  $A + A = A$
6.  $A + \bar{A} = 1$
7.  $A \cdot A = A$
8.  $A \cdot \bar{A} = 0$
9.  $\bar{\bar{A}} = A$
10.  $A + AB = A$
11.  $A + \bar{A}B = A + B$
12.  $(A + B)(A + C) = A + BC$



$$X = A + A = A$$

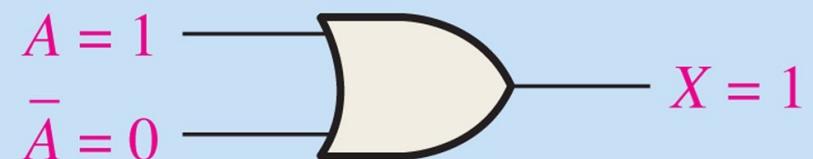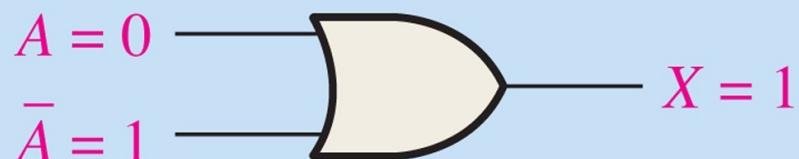

0	0	0
0	1	1
1	0	1
1	1	1

$$X = A + \bar{A} = 1$$

OR

## Rules of Boolean Algebra (7-8)

1.  $A + 0 = A$
2.  $A + 1 = 1$
3.  $A \cdot 0 = 0$
4.  $A \cdot 1 = A$
5.  $A + A = A$
6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$
8.  $A \cdot \bar{A} = 0$
9.  $\bar{\bar{A}} = A$

10.  $A + AB = A$
11.  $A + \bar{A}B = A + B$
12.  $(A + B)(A + C) = A + BC$



$$X = A \cdot A = A$$



$$X = A \cdot \bar{A} = 0$$



0	0	0
0	1	0
1	0	0
1	1	1

AND

## Rules of Boolean Algebra (9)

1.  $A + 0 = A$
2.  $A + 1 = 1$
3.  $A \cdot 0 = 0$
4.  $A \cdot 1 = A$
5.  $A + A = A$
6.  $A + \bar{A} = 1$

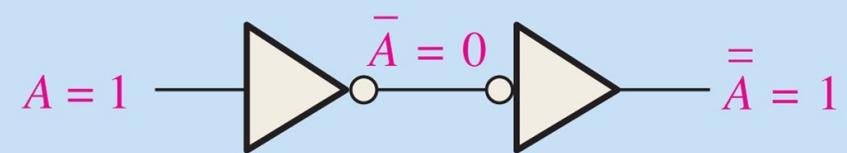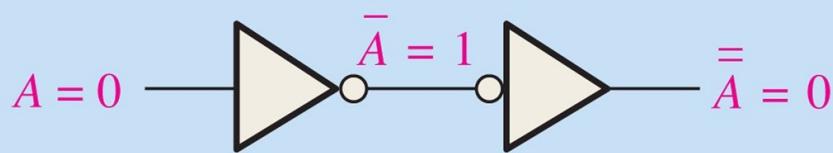7.  $A \cdot A = A$
8.  $A \cdot \bar{A} = 0$
9.  $\bar{\bar{A}} = A$
10.  $A + AB = A$
11.  $A + \bar{A}B = A + B$
12.  $(A + B)(A + C) = A + BC$



$$\bar{\bar{A}} = A$$

# Rules of Boolean Algebra (10)

1.  $A + 0 = A$
2.  $A + 1 = 1$
3.  $A \cdot 0 = 0$
4.  $A \cdot 1 = A$
5.  $A + A = A$
6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$
8.  $A \cdot \bar{A} = 0$
9.  $\bar{\bar{A}} = A$
- 10.  $A + AB = A$**
11.  $A + AB = A + B$
12.  $(A + B)(A + C) = A + BC$

## Regra 10: $A + A \cdot B = A$


<b>A</b>	<b>B</b>	<b>AB</b>	<b><math>A + AB</math></b>
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

iguais

Conexão direta

$$\begin{aligned}
 A + A \cdot B &= A \cdot 1 + A \cdot B \\
 &= A \cdot (1 + B) \\
 &= A \cdot 1 \\
 &= A
 \end{aligned}$$

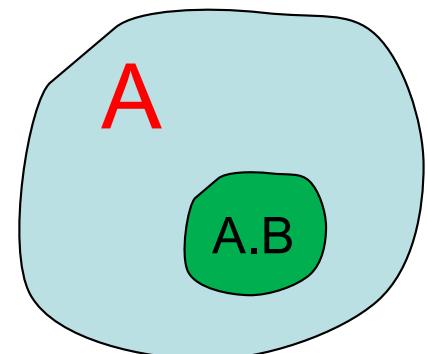Regra 4:  $A \cdot 1 = A$   
 Propriedade Distributiva  
 Regra 2:  $(1 + B) = 1$   
 Regra 4:  $A \cdot 1 = A$




# Rules of Boolean Algebra (11)

1.  $A + 0 = A$
2.  $A + 1 = 1$
3.  $A \cdot 0 = 0$
4.  $A \cdot 1 = A$
5.  $A + A = A$
6.  $A + \bar{A} = 1$
7.  $A \cdot A = A$
8.  $A \cdot \bar{A} = 0$
9.  $\bar{\bar{A}} = A$
10.  $A + AB = A$
- 11.  $A + \bar{A}B = A + B$**
12.  $(A + B)(A + C) = A + BC$

Regra 11:  $A + \bar{A}B = A + B$

$A$	$B$	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1


$\uparrow$  iguais  $\uparrow$

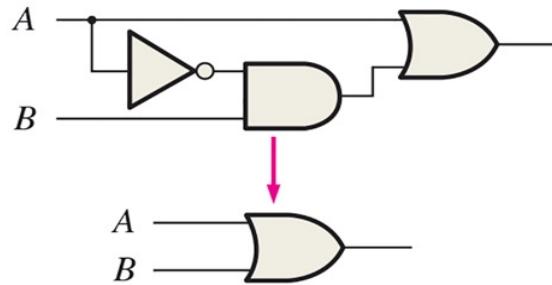

$$\begin{aligned}
 A + \bar{A}B &= (A + A \cdot B) + \bar{A} \cdot B \\
 &= A + A \cdot B + \bar{A} \cdot B \\
 &= A + B \cdot (A + \bar{A}) \\
 &= A + B
 \end{aligned}$$

Regra 10:  $A = A + A \cdot B$

Regra 6:  $A + \bar{A} = 1$

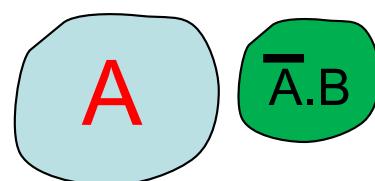

## Rules of Boolean Algebra (12)

- |  |  |
|--|--|
| <ol style="list-style-type: none"> <li>1. <math>A + 0 = A</math></li> <li>2. <math>A + 1 = 1</math></li> <li>3. <math>A \cdot 0 = 0</math></li> <li>4. <math>A \cdot 1 = A</math></li> <li>5. <math>A + A = A</math></li> <li>6. <math>A + \bar{A} = 1</math></li> </ol> | <ol style="list-style-type: none"> <li>7. <math>A \cdot A = A</math></li> <li>8. <math>A \cdot \bar{A} = 0</math></li> <li>9. <math>\bar{\bar{A}} = A</math></li> <li>10. <math>A + AB = A</math></li> <li>11. <math>A + \bar{A}B = A + B</math></li> <li><b>12. <math>(A + B)(A + C) = A + BC</math></b></li> </ol> |
|--|--|

Regra 12:  $(A + B) \cdot (A + C) = A + B \cdot C$

$$(A + B) \cdot (A + C) = A \cdot A + A \cdot C + A \cdot B + B \cdot C$$

# Propriedade Distributiva

$$= A + A \cdot C + A \cdot B + B \cdot C$$

## Regra 7: $A \cdot A = A$

$$= A.(1 + C + B) + B.C$$

## Propriedade Distributiva

$$= A \cdot 1 + B \cdot C$$

## Regra 2: A + 1 = 1

$$= A + B.C$$


## Regra 4: A.1 = A

# TEOREMAS DE DEMORGAN

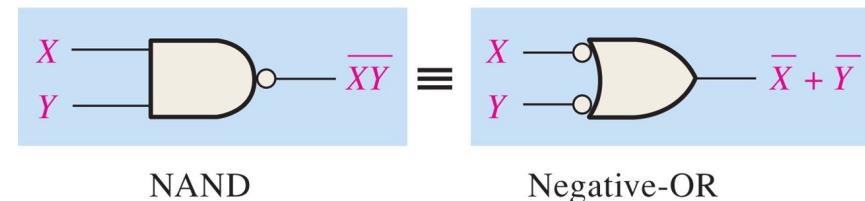
## OBJETIVO DE APLICAR DEMORGAN:

- ✓ Remover a inversão sobre um conjunto de literais.

Abaixo é mostrado as **portas equivalentes** e as correspondentes **tabelas verdade** que ilustram os **Teoremas de DeMorgan**. Observe a igualdade das duas colunas de saída em cada tabela. Isso mostra que as portas equivalentes executam a mesma função lógica.



Inputs		Output	
X	Y	$\overline{XY}$	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

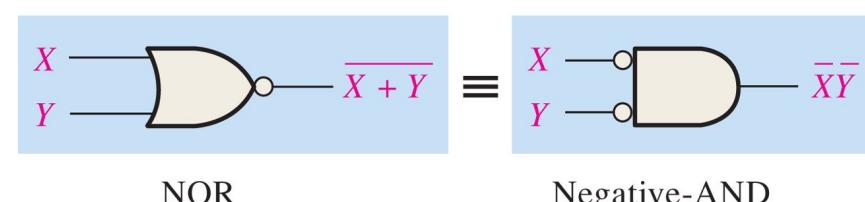


Inputs		Output	
X	Y	$\overline{X + Y}$	$\overline{\overline{XY}}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

## TEOREMAS DE DEMORGAN

Exemplo: Aplique o **Teorema de DeMorgan** para remover a negação que cobre ambos os termos da expressão:  $X = \overline{\overline{C} + D}$

- ✓ Para aplicar o **Teorema de DeMorgan** à expressão, você pode remover a negação que cobre ambos os termos e alterar o sinal entre os termos:

$$X = \overline{\overline{C} + D}$$

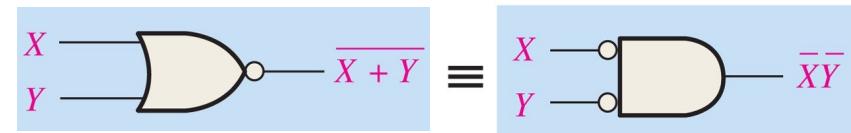

$$X = \overline{\overline{C}} \cdot \overline{\overline{D}}$$

Remove negação dupla

$$X = C \cdot \overline{D}$$

## DeMorgan's Theorem

Apply DeMorgan's theorems to the expressions  $\overline{XYZ}$  and  $\overline{X + Y + Z}$ .

### Solution

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{X + Y + Z} = \overline{X}\overline{Y}\overline{Z}$$

Apply DeMorgan's theorems to the expressions  $\overline{WXYZ}$  and  $\overline{W + X + Y + Z}$ .

### Solution

$$\overline{WXYZ} = \overline{W} + \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{W + X + Y + Z} = \overline{W}\overline{X}\overline{Y}\overline{Z}$$

## DeMorgan's Theorem

### Applying DeMorgan's Theorems

The following procedure illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + B \cdot \bar{C}}} + D \cdot (\overline{E + \bar{F}})$$

$$(\overline{\overline{A + B \cdot \bar{C}}}) \cdot (\overline{D \cdot (\overline{E + \bar{F}})}) \quad \text{Substitui por and}$$

$$(A + B \cdot \bar{C}) \cdot (\bar{D} + \overline{\overline{(E + \bar{F})}}) \quad \text{DeMorgan do segundo termo}$$

$$(A + B \cdot \bar{C}) \cdot (\bar{D} + E + \bar{F}) \quad \text{Pronto, todos literais isolados}$$

## DeMorgan's Theorem

Apply DeMorgan's theorems to each of the following expressions:


(a)  $\overline{(A + B + C)D}$

(b)  $\overline{ABC + DEF}$

(c)  $\overline{AB} + \overline{CD} + EF$

# SIMPLIFICAÇÃO LÓGICA USANDO ÁLGEBRA BOOLEANA

Simplify this expression  $AB + A(B + C) + B(B + C)$

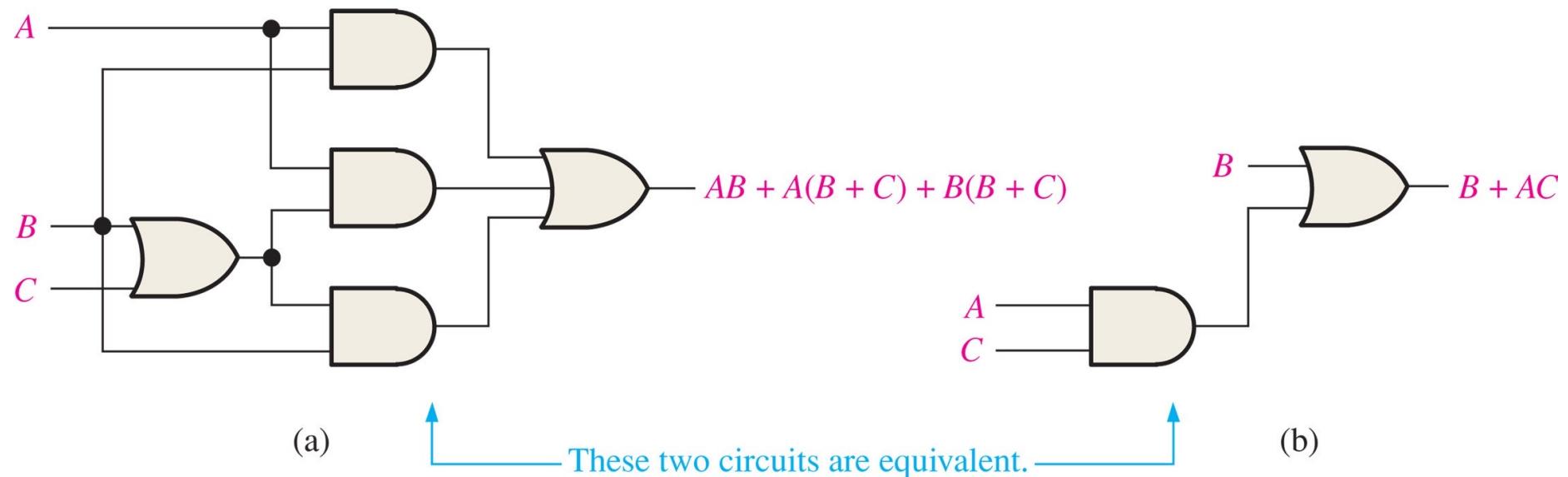

**FIGURE 4-20** Gate circuits for Example 4-9.

Solução próximo slide

## Logic Simplification Using Boolean Algebra


Simplify this expression  $AB + A(B + C) + B(B + C)$

**Step 1:** Apply the distributive law to the second and third terms in the expression, as follows:

$$AB + AB + AC + BB + BC$$


**Step 2:** Apply rule 7 ( $BB = B$ ) to the fourth term.

$$AB + AB + AC + \boxed{B} + BC$$

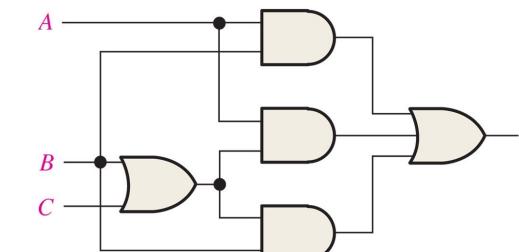

$$B + B.(qq\ cosa) = B$$

$$B + AC$$

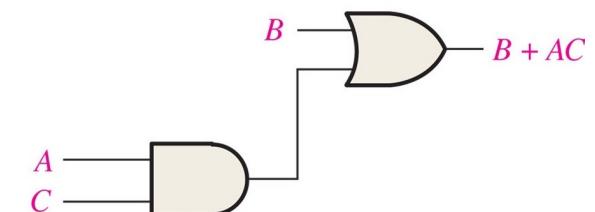

# MINIMIZAR

Simplify this expression  $[AB'(C + BD) + A' \cdot B'] \cdot C$

(p.206)

Solution:  $B' \cdot C$

# MINIMIZAR 1/4

$$F = B.C.D.E + B.C.(\overline{D.E}) + (\overline{B.C}).D.E$$

$$F = B.C.D.[B.C + \overline{D}.(C.D + B.D)]$$

$$F = \overline{B}.\overline{C}.D + \overline{(B+C+D)} + \overline{B}.\overline{C}.\overline{D}.E$$

# MINIMIZAR 2/4

$$F = C \cdot E + C \cdot (E + F) + \bar{E} \cdot (E + G)$$

$$F = (C + CD) \cdot (C + \bar{C}D)(C + E)$$

# MINIMIZAR 3/4

**Exercise 2.7** Simplify the following Boolean equations using Boolean theorems.  
Check for correctness using a truth table or K-map.

$$(a) \quad Y = AC + \overline{A}\overline{B}C = \textcolor{red}{AC + AB'C + A'B'C} = \textcolor{red}{AC + B'C}$$

$$(b) \quad Y = \overline{A}\overline{B} + \overline{A}B\overline{C} + \overline{(A + \overline{C})}$$

$$(c) \quad Y = \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C} + A\overline{B}C\overline{D} + ABD + \overline{A}\overline{B}C\overline{D} + B\overline{C}D + \overline{A}$$

$$10. \quad A + AB = A$$

$$11. \quad A + \overline{A}B = A + B$$

$$(b) \quad = \textcolor{red}{A'B' + A'BC' + A'C} = A' (B' + BC' + C) = A' (B' + C' + C) = A'$$

$$(c) \quad Y = \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C} + A\bar{B}C\bar{D} + ABD + \bar{A}\bar{B}C\bar{D} + B\bar{C}D + \bar{A}$$

Tirar o A de onde não precisa

$$Y = \bar{B}.\bar{C} + \bar{B}.C.\bar{D} + B.D + B.\bar{C}.D + \bar{A}$$

$$Y = \bar{B}.\bar{C} + \bar{B}.C.\bar{D} + B.D + B.\bar{C}.D + \bar{A}$$

$$Y = \bar{B}.\bar{C} + \bar{B}.C.\bar{D} + B.D + \bar{A}$$

$$Y = \bar{B}.(\bar{C} + C.\bar{D}) + B.D + \bar{A}$$

$$Y = \bar{B}.(\bar{C} + \bar{D}) + B.D + \bar{A}$$



$$Y = \bar{B}.\bar{C} + \bar{B}.\bar{D} + B.D + \bar{A}$$

# MINIMIZAR 4/4

$$F = \overline{A \cdot B + A \cdot C} + A \cdot \overline{B} \cdot C$$

- Simplifique a expressão acima utilizando as regras de álgebra Booleana. Explicar o procedimento.
- Desenhe o circuitos lógicos correspondentes à expressão acima e ao circuito lógico minimizado.
- Apresente a tabela verdade da função, E apresentar a função na forma de um somatório de mintermos.
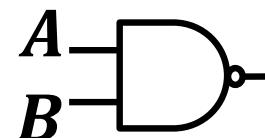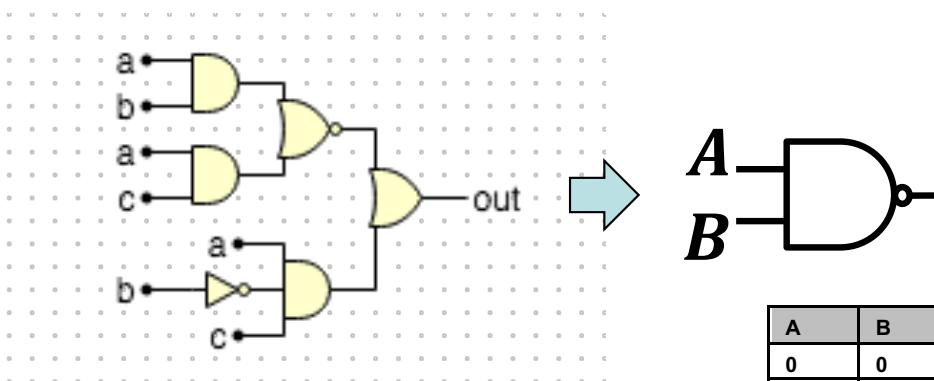
$$\begin{aligned} F &= \overline{A \cdot B + A \cdot C} + A \cdot \overline{B} \cdot C = (\overline{A} + \overline{B}) \cdot (\overline{A} + \overline{C}) + A \cdot \overline{B} \cdot C \\ &= \overline{A} + \overline{B} \cdot \overline{C} + A \cdot \overline{B} \cdot C \\ &= \overline{A} + \overline{B} \cdot \overline{C} + \overline{B} \cdot C \\ &= \overline{A} + \overline{B} \end{aligned}$$



A	B	C	F	mintermos
0	0	0	1	0
0	0	1	1	1
0	1	0	1	2
0	1	1	1	3
1	0	0	1	4
1	0	1	1	5
1	1	0		
1	1	1		

$$F(A, B, C) = \sum(0, 1, 2, 3, 4, 5)$$

# De Morgan

$$F = \overline{A \cdot \bar{B} \cdot (C + \bar{D})}$$

$$\overline{\overline{AB}(C + \bar{D})} = \overline{\overline{AB}} + \overline{(C + \bar{D})} = \overline{A} + \overline{B} + \overline{C}\overline{D}$$

$$F = \overline{(\overline{A} + B + C + D)} \cdot \overline{(A \cdot \bar{B} \cdot \bar{C} \cdot D)}$$

$$\overline{\overline{\overline{A} + B + C + D}} \cdot \overline{\overline{\overline{ABC}D}} = (\overline{\overline{ABC}D})(\overline{A} + B + C + \overline{D})$$

$$\overline{\overline{ABC}D} + \overline{\overline{A} + B + C + \overline{D}} = \overline{A} + B + C + D + \overline{ABC}D$$

$$F = \overline{A + \overline{B \cdot \bar{C}} + C \cdot D + \overline{B \cdot \bar{C}}}$$

$$(A + \overline{\overline{BC}} + CD) + \overline{\overline{BC}} = \overline{A}(\overline{BC})(\overline{CD}) + BC = \overline{A}(\overline{BC})(\overline{CD}) + BC$$

$$\overline{ABC}(\overline{C} + \overline{D}) + BC = \overline{ABC} + \overline{ABC}\overline{D} + BC = \overline{ABC}(1 + \overline{D}) + BC$$

$$\overline{ABC} + BC$$

## FORMATO DAS EXPRESSÕES BOOLEANAS

- Boolean expressions can be written in the **sum-of-products** form (**SOP**) or in the **product-of-sums** form (**POS**)
  - These forms can simplify the implementation of combinational logic
  - In both forms, an overbar cannot extend over more than one variable
- An expression is in SOP form when two or more product terms are summed as in the following examples

$$\overline{A} \overline{B} \overline{C} + AB$$

$$AB\overline{C} + \overline{C}\overline{D}$$

$$CD + \overline{E}$$



- An expression is in POS form when two or more sum terms are multiplied as in the following examples:

$$(A + B)(\overline{A} + C)$$


$$(A + B + \overline{C})(B + D)$$

$$(\overline{A} + B)C$$

**FIGURE 4-22** Implementation of the SOP expression  $AB + BCD + AC$ .

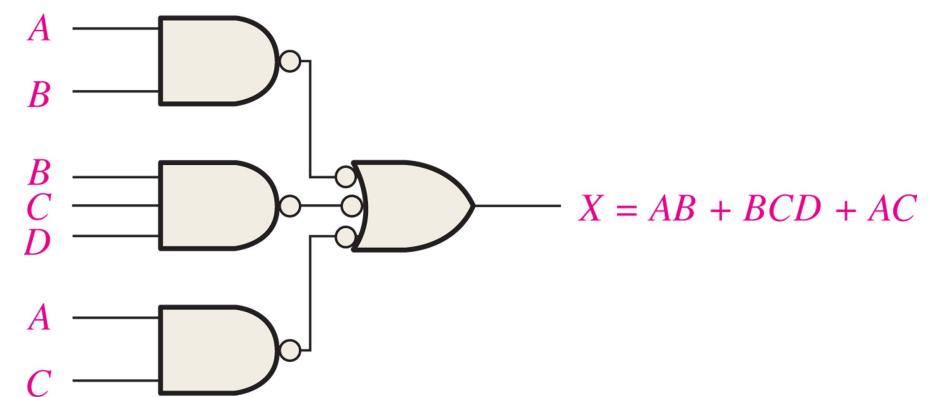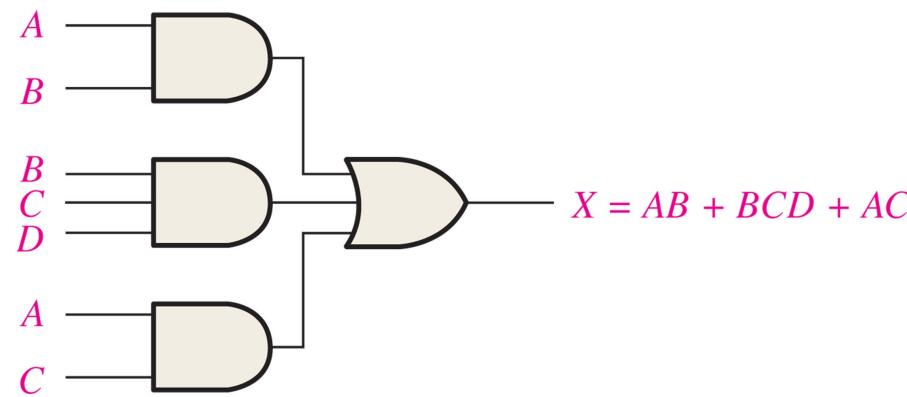

**FIGURE 4-24** Implementation of the POS expression  $(A + B)(B + C + D)(A + C)$ .

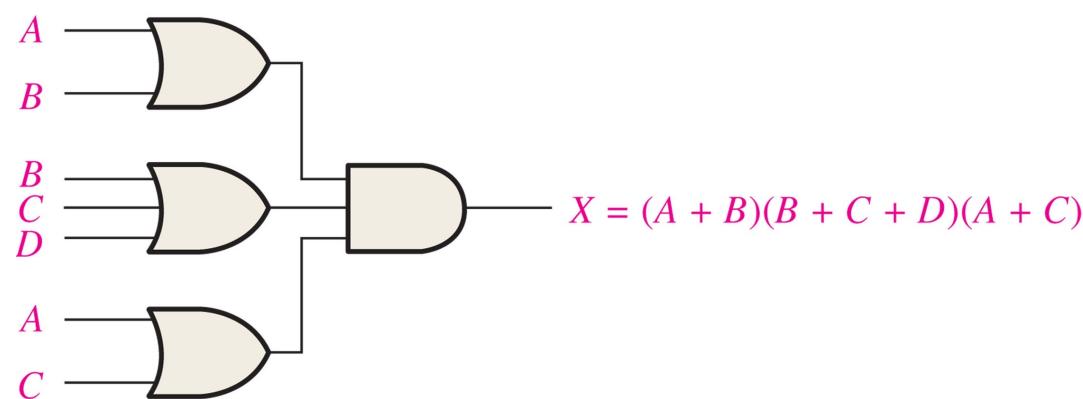

## Standard Forms of Boolean Expressions

- In **SOP standard form**, every variable in the domain must appear in each term
- You can expand a **nonstandard** term to **standard** form by multiplying the term by a term consisting of the sum of the missing variable and its complement
- Convert  $X = \bar{A} \bar{B} + A B C$  to standard form:

The first term does not include the variable  $C$ . Therefore, multiply it by the  $(C + \bar{C})$ , which = 1:

$$\begin{aligned} X &= \bar{A} \bar{B} (C + \bar{C}) + A B C \\ &= \bar{A} \bar{B} C + \bar{A} \bar{B} \bar{C} + A B C \end{aligned}$$

# Standard Forms of Boolean Expressions

## EXAMPLE 4-15

Convert the following Boolean expression into standard SOP form:

$$A\bar{B}C + \bar{A}\bar{B} + A\bar{B}CD$$

### EXAMPLE 4-15

Convert the following Boolean expression into standard SOP form:

$$A\bar{B}C + \bar{A}\bar{B} + A\bar{B}CD$$

#### Solution

The domain of this SOP expression is  $A, B, C, D$ . Take one term at a time. The first term,  $A\bar{B}C$ , is missing variable  $D$  or  $\bar{D}$ , so multiply the first term by  $D + \bar{D}$  as follows:

$$A\bar{B}C = A\bar{B}C(D + \bar{D}) = A\bar{B}CD + A\bar{B}C\bar{D}$$

In this case, two standard product terms are the result.

The second term,  $\bar{A}\bar{B}$ , is missing variables  $C$  or  $\bar{C}$  and  $D$  or  $\bar{D}$ , so first multiply the second term by  $C + \bar{C}$  as follows:

$$\bar{A}\bar{B} = \bar{A}\bar{B}(C + \bar{C}) = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$$

The two resulting terms are missing variable  $D$  or  $\bar{D}$ , so multiply both terms by  $D + \bar{D}$  as follows:

$$\begin{aligned} \bar{A}\bar{B} &= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} = \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} \\ &= \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D \end{aligned}$$

In this case, four standard product terms are the result.

The third term,  $A\bar{B}CD$ , is already in standard form. The complete standard SOP form of the original expression is as follows:

$$A\bar{B}C + \bar{A}\bar{B} + A\bar{B}CD = A\bar{B}CD + A\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$$

$$Y = A.\bar{B}.C.x + \bar{A}.\bar{B}.x.x + A.B.\bar{C}.D$$

10/11      0/1/2/3      13

$$= A\bar{B}CD + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + AB\bar{C}D$$


11      10      3      2      1      0      13

$$Y = \Sigma(0, 1, 2, 3, 10, 11, 13)$$

## Truth Table → SOP

**TABLE 4-8**

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

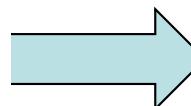


$$011 \longrightarrow \bar{A}BC$$

$$100 \longrightarrow A\bar{B}\bar{C}$$

$$110 \longrightarrow AB\bar{C}$$


$$111 \longrightarrow ABC$$

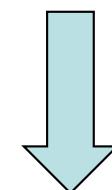

$$X = A'BC + AB'C' + ABC' + ABC$$

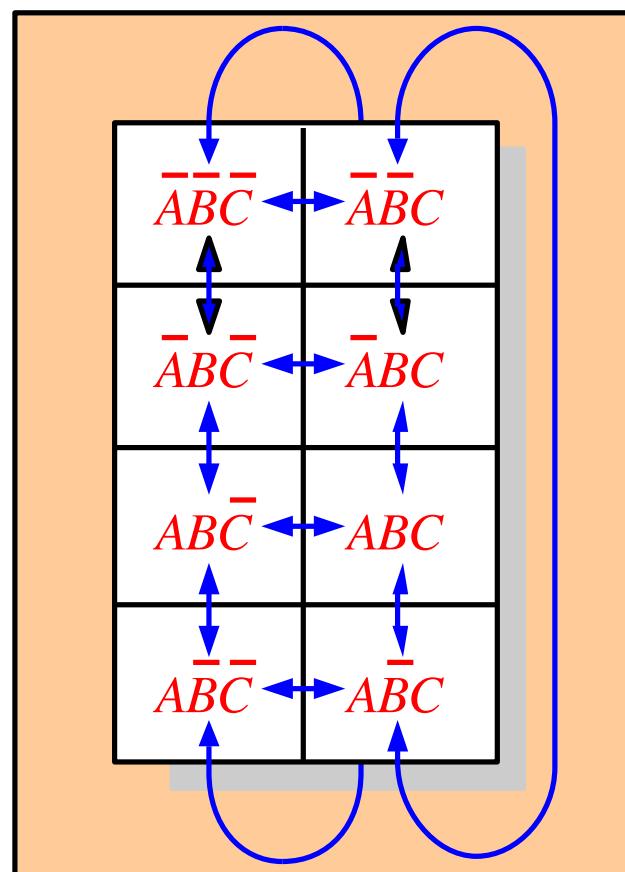
## Karnaugh maps

- O mapa de Karnaugh é um método para simplificar a lógica combinacional com até 6 variáveis. Para 3 variáveis, 8 células são necessárias ( $2^3$ )
- Cada célula difere de uma célula adjacente por apenas uma variável**
- O mapa mostrado abaixo é para três variáveis denominadas como A, B e C. Cada célula representa minitermo




$AB \backslash C$	0	1
00	0	1
01	2	3
11	6	7
10	4	5

## Karnaugh maps

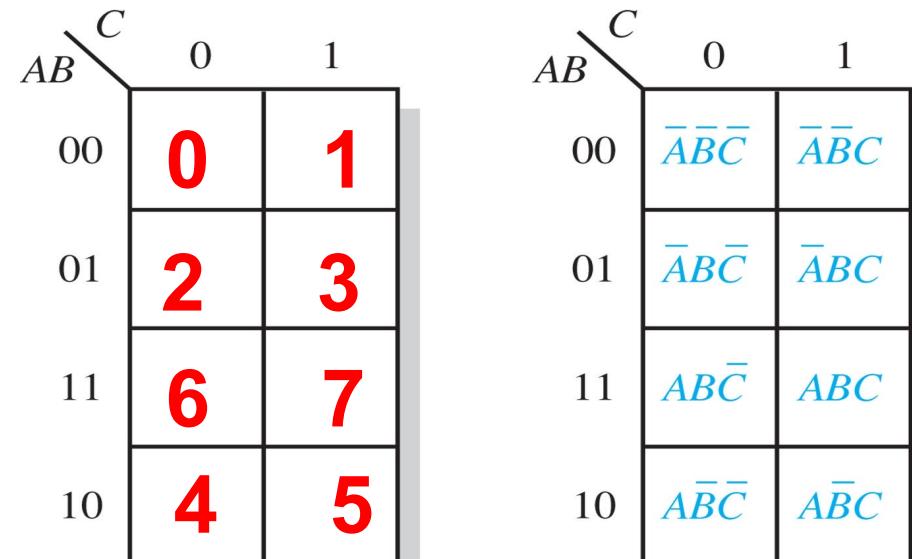

## TABELA VERDADE E MAPA DE KARNAUGH

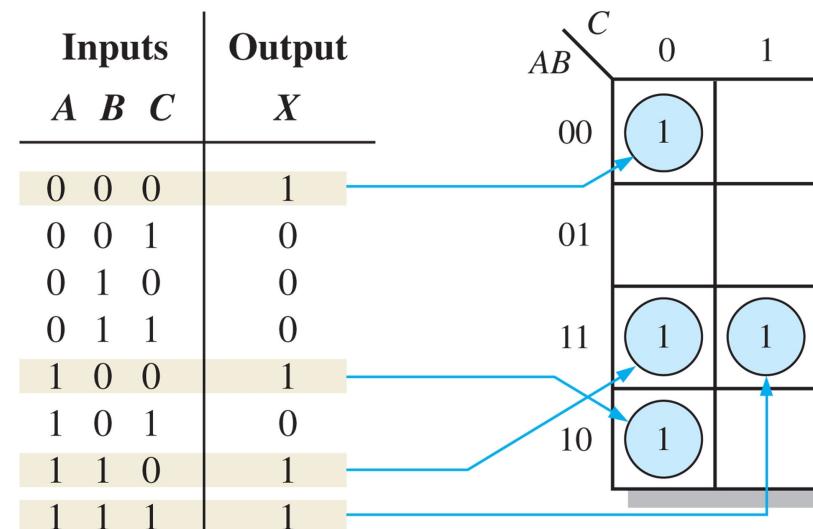


**FIGURE 4-25** A 3-variable Karnaugh map showing Boolean product terms for each cell.

## Karnaugh maps

K-maps podem simplificar a lógica combinacional agrupando células e ***eliminando variáveis redundantes***

$$A \cdot B + A \cdot \bar{B} = A$$

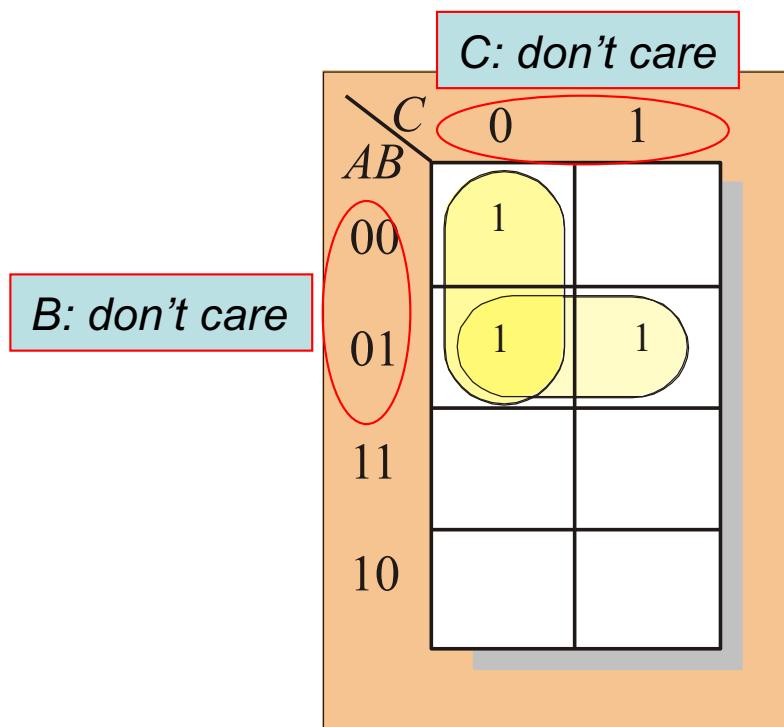1. Agrupar os 1's em grupos de 2/4/8 mintermos
2. Eliminar as variáveis redundantes
3. O grupo vertical é lido como:  $\bar{A} \cdot \bar{C}$
4. O grupo horizontal é lido como:  $\bar{A} \cdot B$



$$X = \bar{A} \cdot \bar{C} + \bar{A} \cdot B$$


## Minimize (1/5)

38

**FIGURE 4-39** Example of mapping directly from a truth table to a Karnaugh map.

$$X = \overline{ABC} + \overline{AB}\overline{C} + A\overline{B}\overline{C} + ABC$$

Inputs			Output
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
4	1	0	1
1	0	1	0
6	1	1	0
7	1	1	1

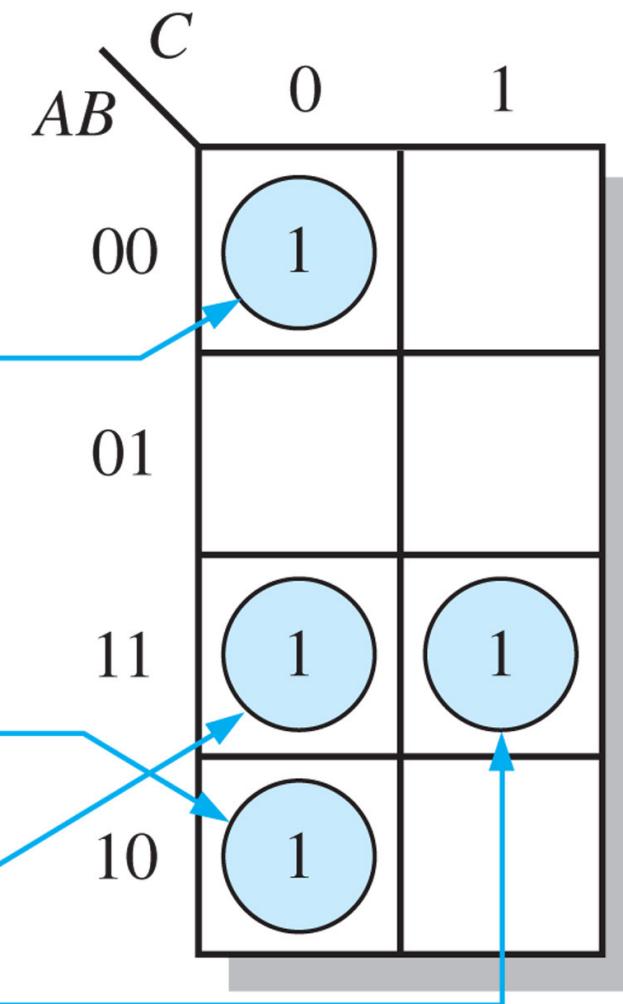


## Minimize (1/5)

39

FIGURE 4-39 Example of mapping directly from a truth table to a Karnaugh map.
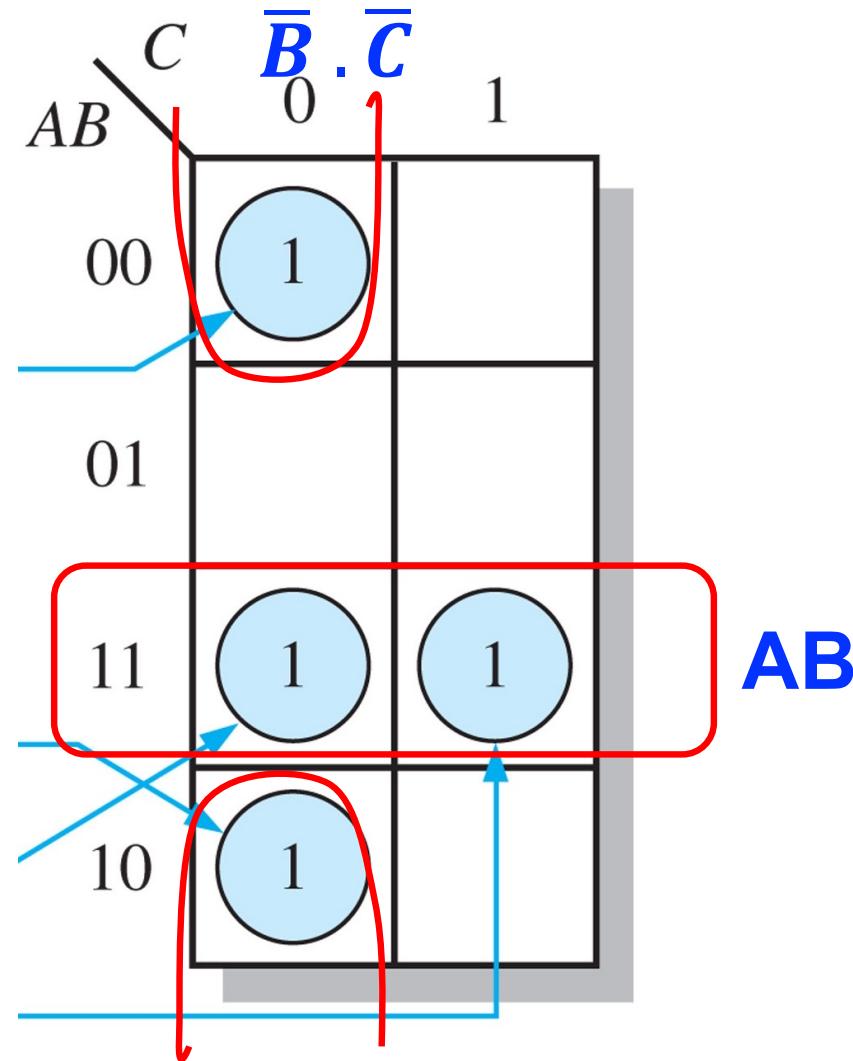
$$X = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + ABC$$



$$X = \overline{B}.\overline{C} + A.B$$

## Minimize (2/5)

		$Y \cdot Z$				
		00	01	11	10	
X		0	0	0	1	0
$X \cdot \bar{Z}$		1	0	1	1	

$$F = \Sigma(3, 4, 6, 7)$$

$$F = Y \cdot Z + X \cdot \bar{Z}$$

		$Y \cdot Z$				
		00	01	11	10	
X		0	m0	m1	m3	m2
1		1	m4	m5	m7	m6

$$\begin{array}{l} m2 + m3 + m6 + m7 \\ \downarrow \quad \downarrow \\ \bar{X}Y \quad XY \end{array}$$

É o que há de comum entre os 4 mintermos

$$= (\bar{X} + X) Y = Y$$

## Minimize (3/5)

41


$$F = \sum(0, 1, 2, 3, 4, 5, 6) = \prod(7)$$

$$F = \bar{A} + \bar{B} + \bar{C}$$

Using maxterms:

$$\bar{F} = A \cdot B \cdot C$$





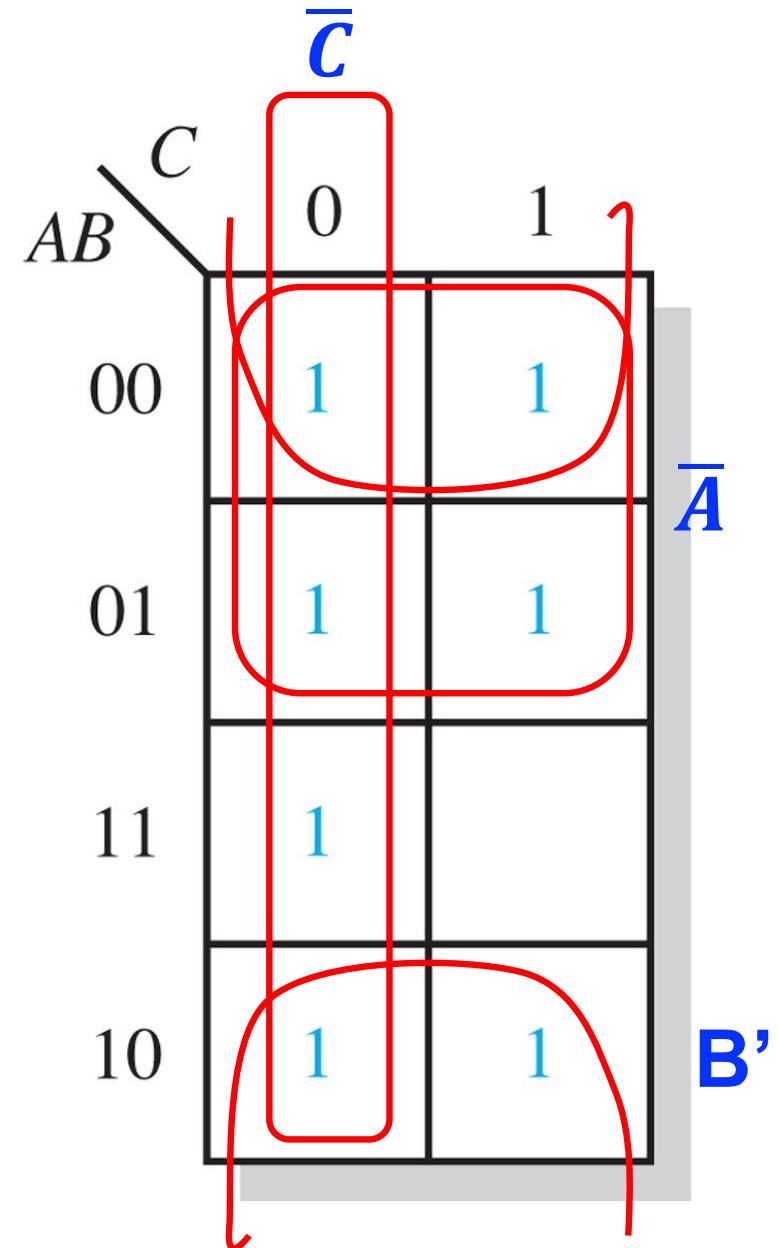
De Morgan:  $F = \bar{A} + \bar{B} + \bar{C}$



## Minimize (4/5)

FIGURE 4-33

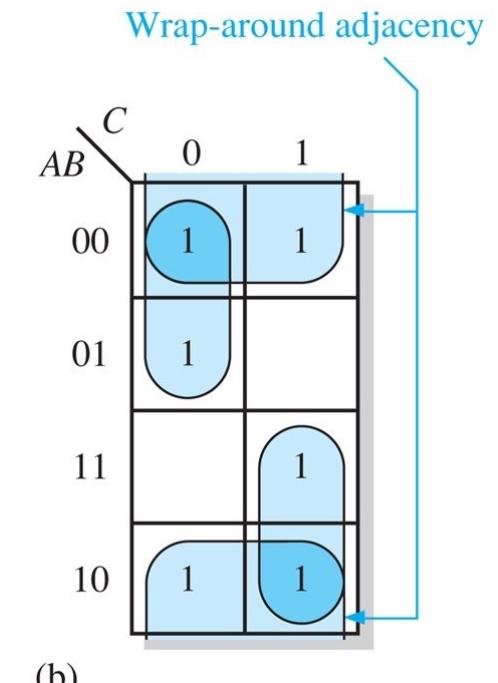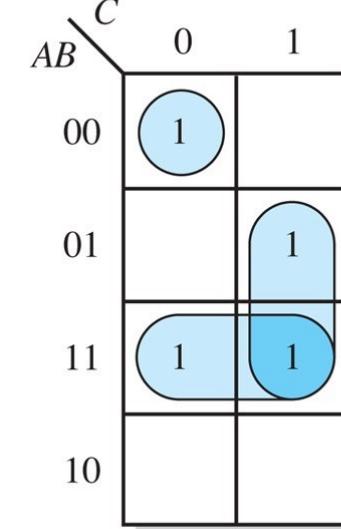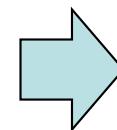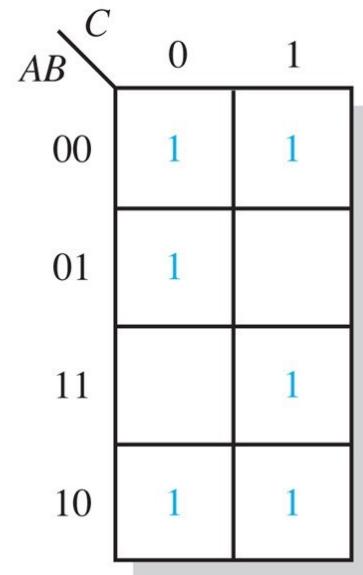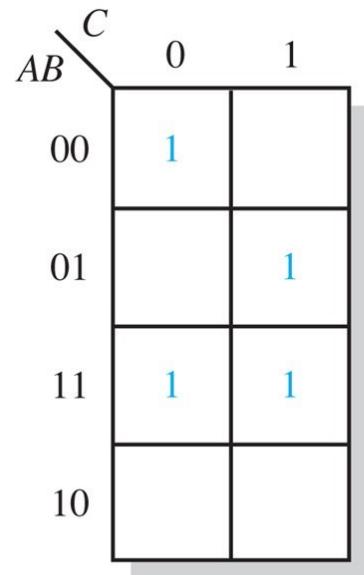Como agrupar? Qual a função minimizada resultante?



$$(a) F = AB + BC + \bar{A} \cdot \bar{B} \cdot \bar{C}$$



$$(b) F = \bar{A} \cdot \bar{C} + A \cdot C + \bar{B}$$

## Minimize (4/5)

43

FIGURE 4-33

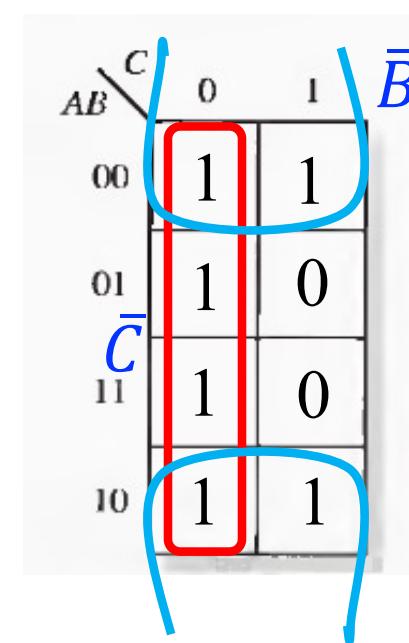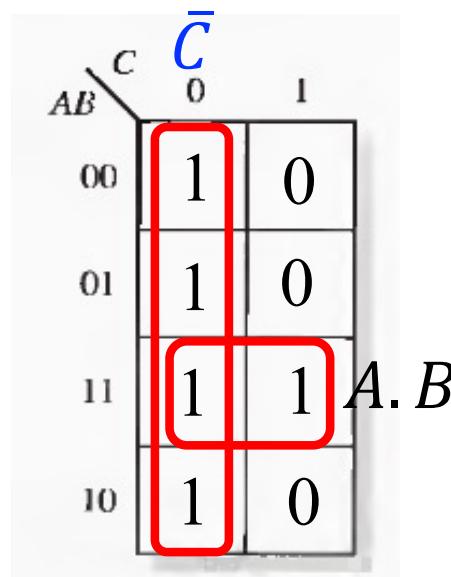Como agrupar? Qual a função minimizada resultante?



## Minimize (5/5)


Determine the functions:

- $F1 = \sum (0,1,7,6)$
- $F2 = \sum (0,2,3,4,6,7)$

A \ BC	00	01	11	10
0				
1				

A \ BC	00	01	11	10
0	1	1		
1			1	1
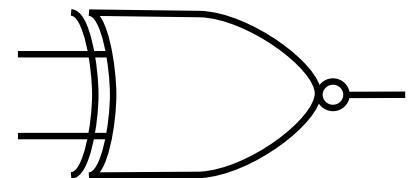
$$F1 = \bar{A} \cdot \bar{B} + A \cdot B$$



A \ BC	00	01	11	10
0	1		1	1
1	1		1	1


$$F2 = B + \bar{C}$$

$$\overline{F2} = \bar{B} \cdot C$$

(aplica de Morgam e obtém F2)

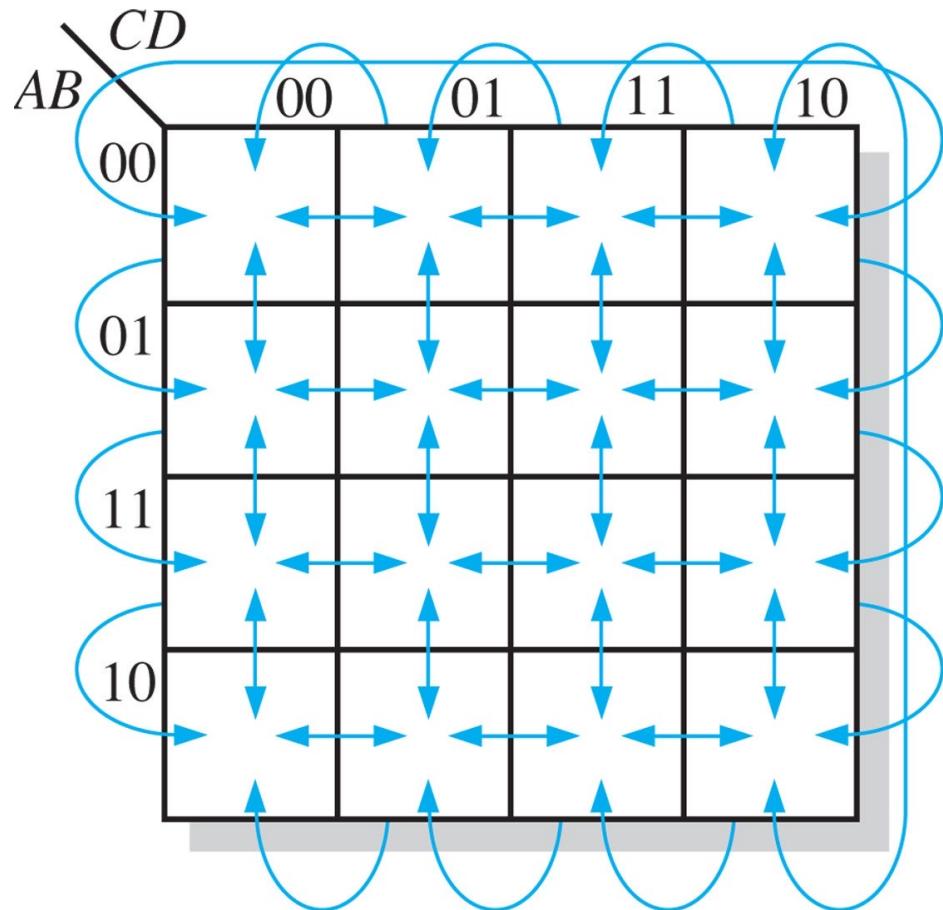
## Karnaugh maps – 4 variables

A 4-variable map has an adjacent cell on each of its four boundaries




Each cell is different only by one variable from an adjacent cell

**FIGURE 4-26** A 4-variable Karnaugh map.

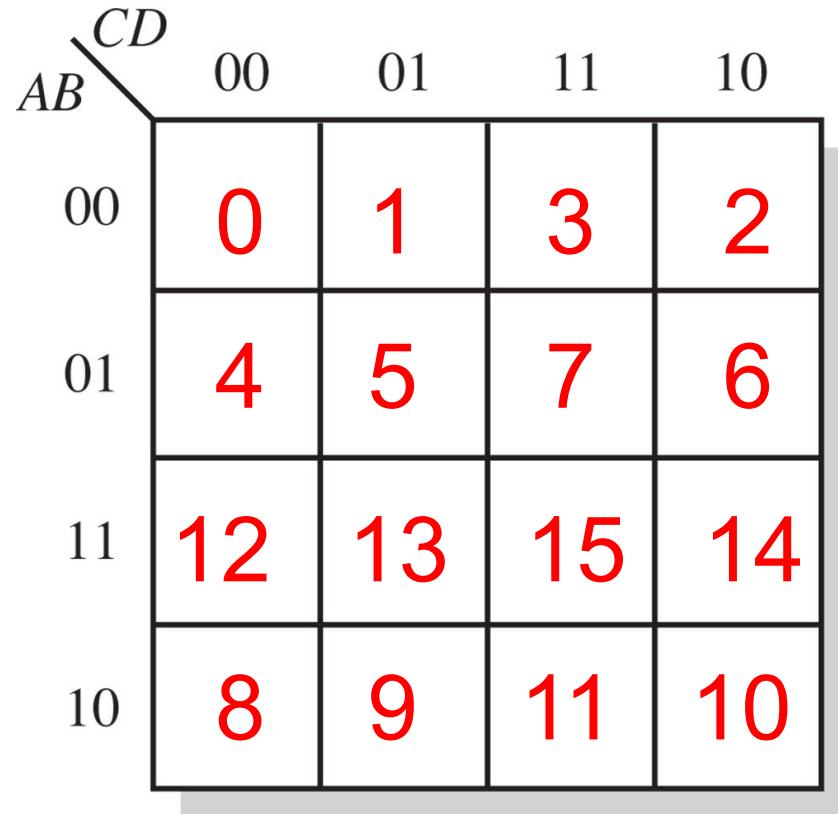


(a)

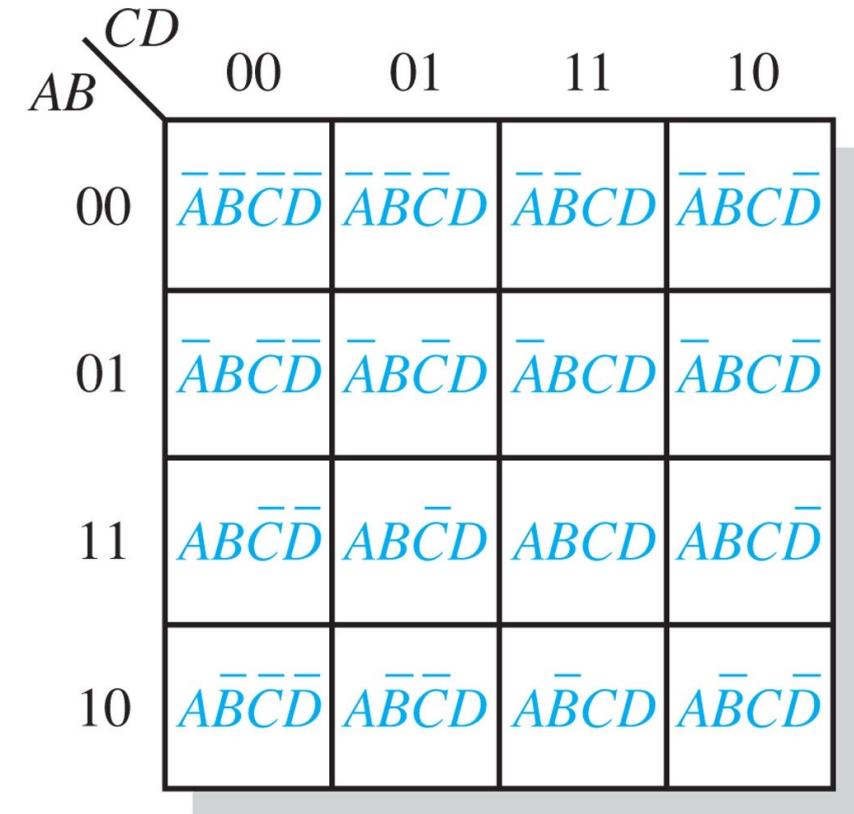

(b)
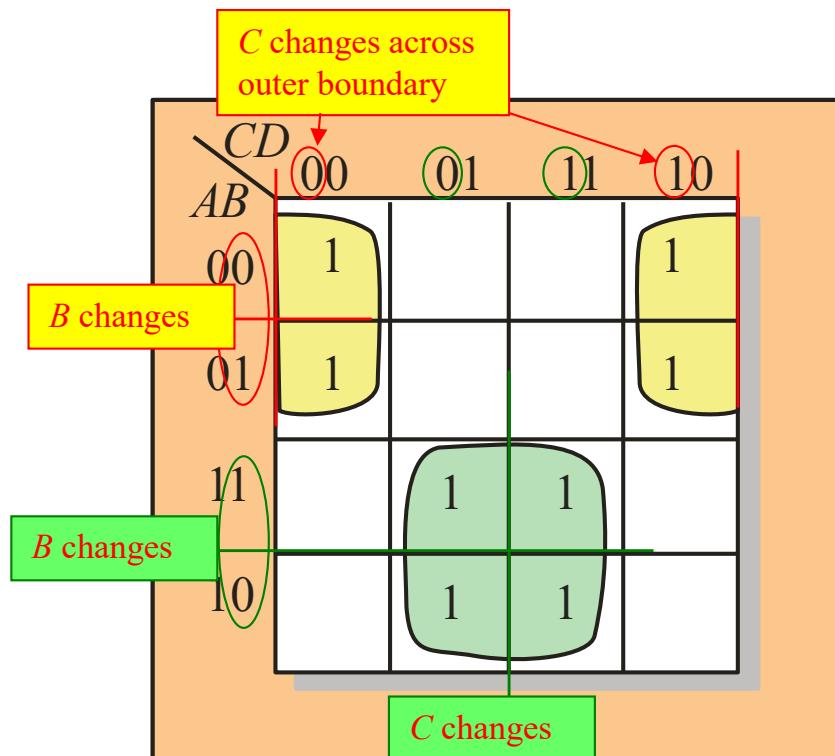
## Karnaugh maps – 4 variables

Agrupar os 1's no K-map de forma a minimizar a função.



1. Agrupe os 1's em dois grupos separados, conforme indicado.
2. Para cada grupo eliminar os literais redundantes.


O grupo amarelo é  $\bar{A} \cdot \bar{D}$

O grupo verde é  $A \cdot D$

$$F = \bar{A} \cdot \bar{D} + A \cdot D$$

Map the following SOP expression on a Karnaugh map:
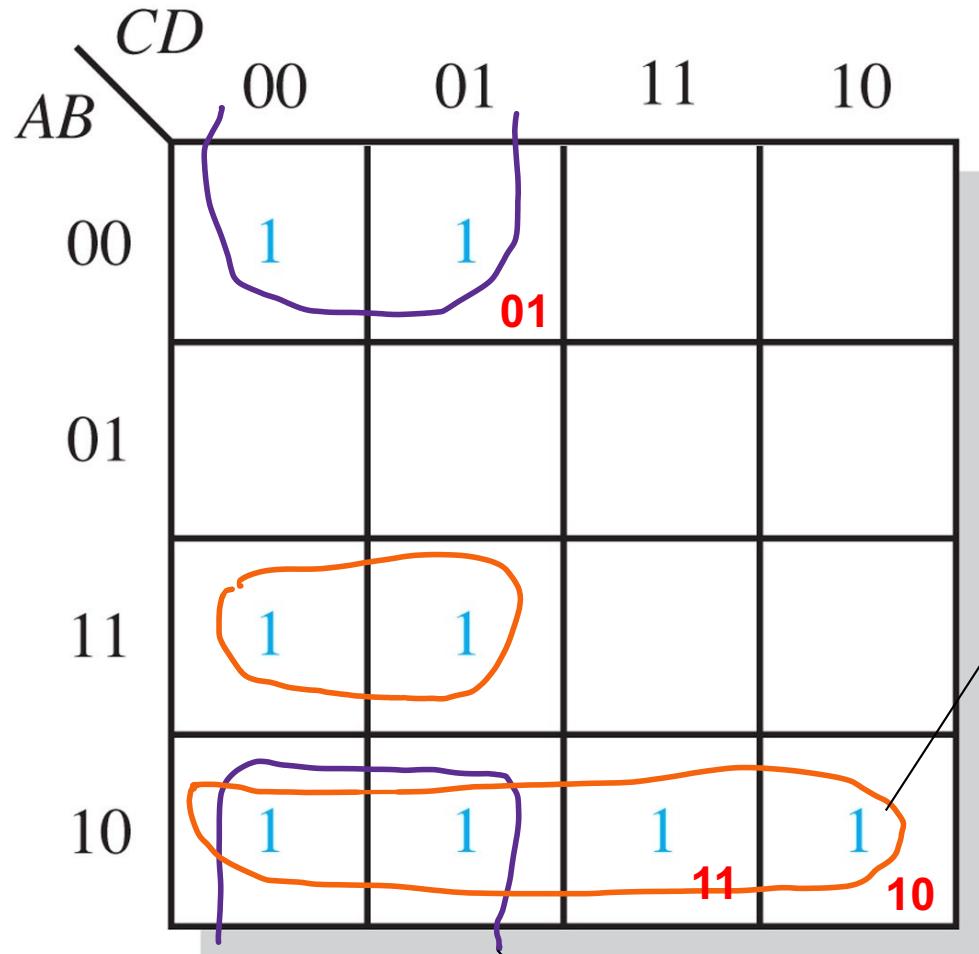
$$F = \underline{B'C'} + \underline{AB} + \underline{ABC'} + \underline{\underline{AB'CD'}} + \underline{A'B'C'D} + \underline{AB'CD}$$



Which is the minimized function?

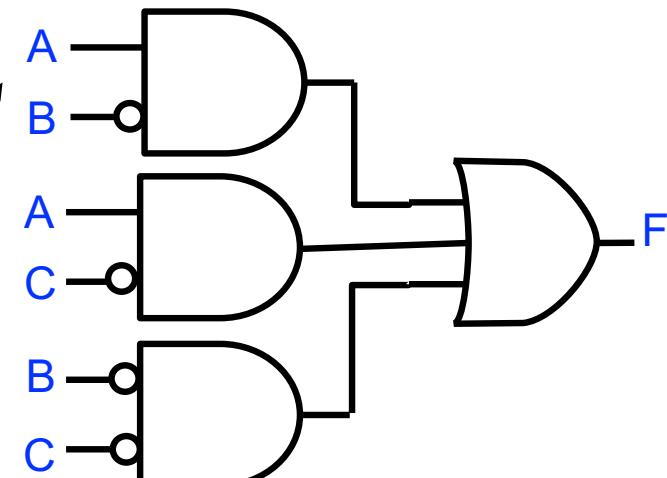


FIGURE 4-32

## Minimizar (2/3)

49

$$F2 = \sum (2, 3, 4, 5, 6, 7, 9, 12, 13, 14, 15)$$

	<i>AB</i>	<i>CD</i>	00	01	11	10
<i>AB</i>	00	00	0	1	3	2
01	01	01	4	5	7	6
11	11	11	12	13	15	14
10	10	10	8	9	11	10

(a)

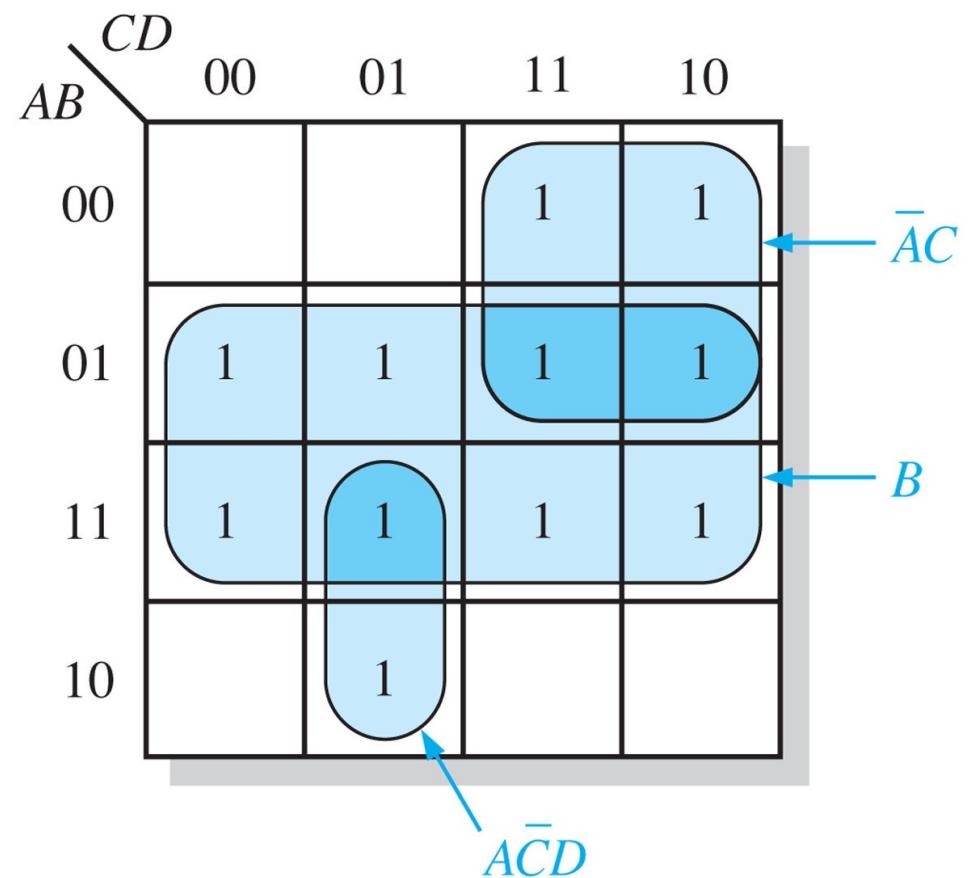


FIGURE 4-35

Mapa de Karnaugh para as seguintes expressões,  
apresentando o circuito resultante

1.  $A'BC + AB'C + AB'C'$
2.  $A'BCD' + ABCD' + ABC'D' + ABCD$

A/BC	00	01	11	10
0			1	
1	1	1		

$$F_1 = AB' + A'BC$$

AB/CD	00	01	11	10
00				
01				1
11		1		1
10				


$$F_2 = ABC + ABD' + BCD'$$

# Uso de don't cares

**FIGURE 4-40** Example of the use of “don’t care” conditions to simplify an expression.

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Don't cares

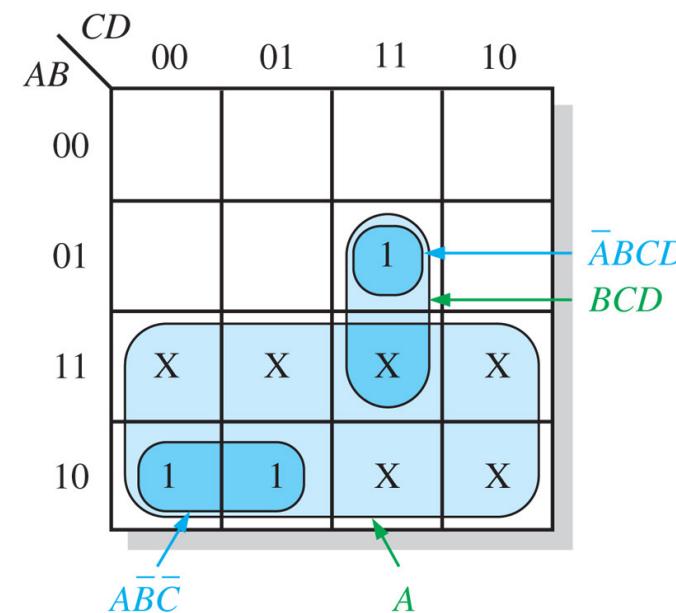


(a) Truth table

(b) Without “don’t care”  $Y = \bar{A}\bar{B}\bar{C} + \bar{A}BCD$   
With “don’t care”  $Y = A + BCD$

## Minimize (4/4) – com don't cares


S <sub>1</sub>	CD	00	01	11	10
AB	00	0	X	0	0
00	01	1	X	X	0
01	11	1	1	X	1
11	10	1	1	X	1
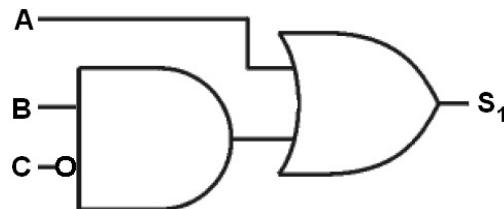
$$S_1 = \textcolor{blue}{B\bar{C}} + \textcolor{red}{A}$$




S <sub>2</sub>	CD	00	01	11	10
AB	00	1	0	0	X
00	01	0	1	X	0
01	11	0	X	1	0
11	10	X	0	0	1
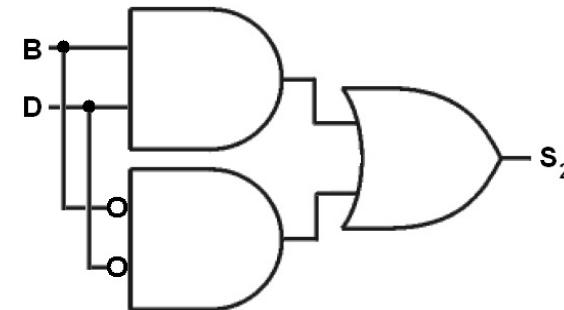
$$S_2 = \textcolor{blue}{BD} + \textcolor{red}{\bar{B}\bar{D}}$$


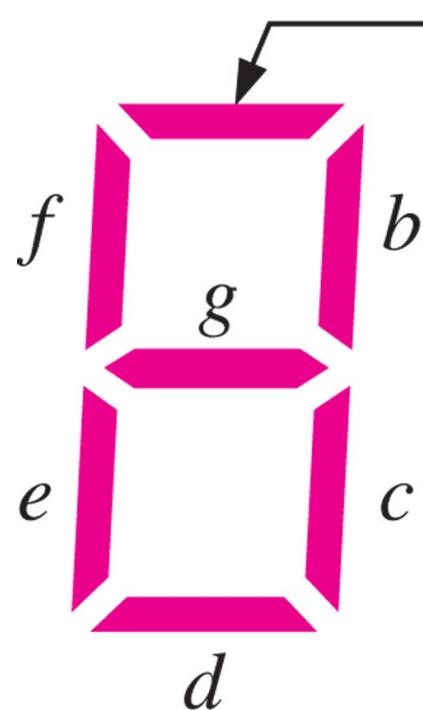
## USO PRÁTICO DE DON'T CARE - BCD para 7 segmentos



Segment *a*

0 2 3 5 6 7 8 9

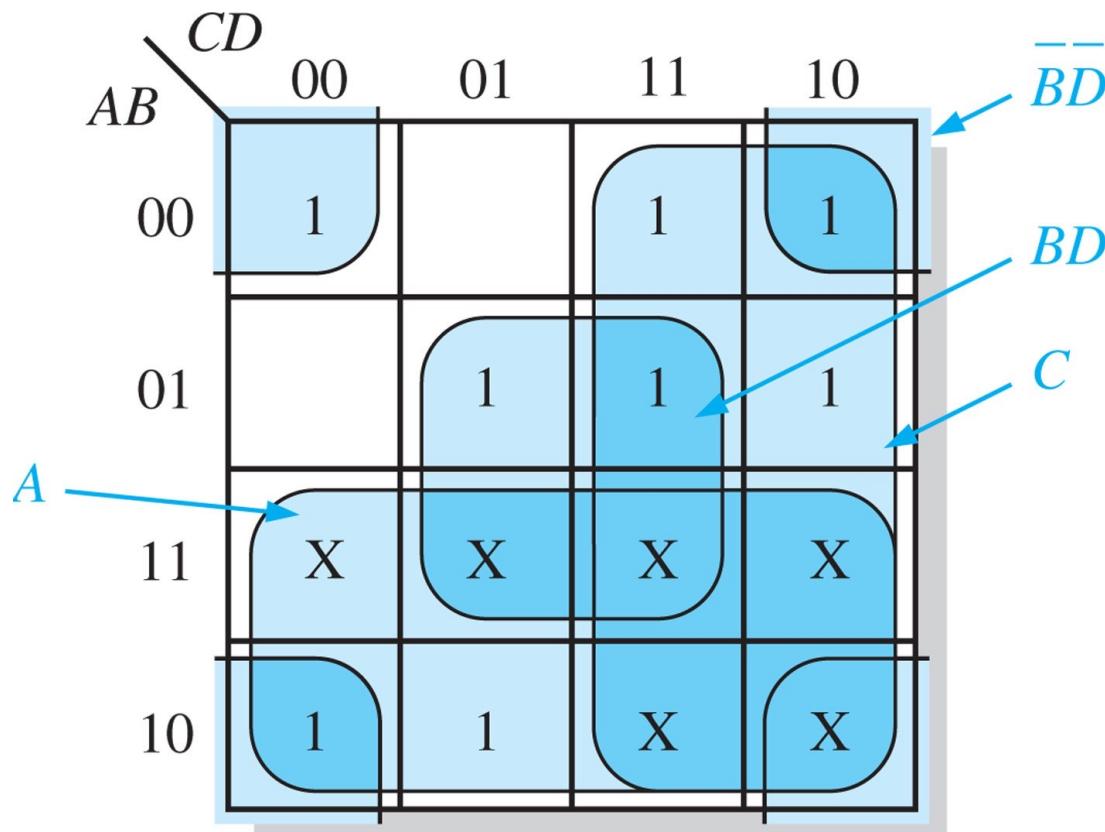


FIGURE 4-41 7-segment display.

FIGURE 4-42

## 2-6 variables

54


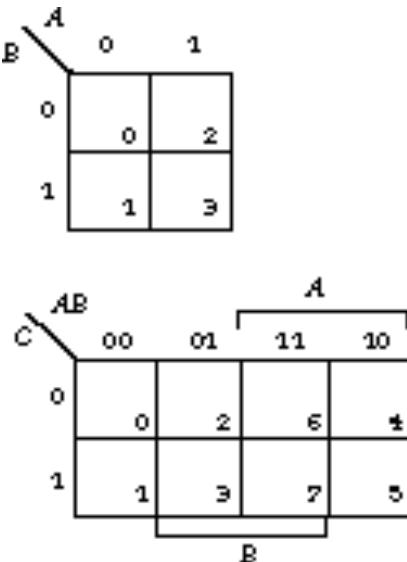



Figure 2.29 Two-, three-, and four-variable K-map templates.

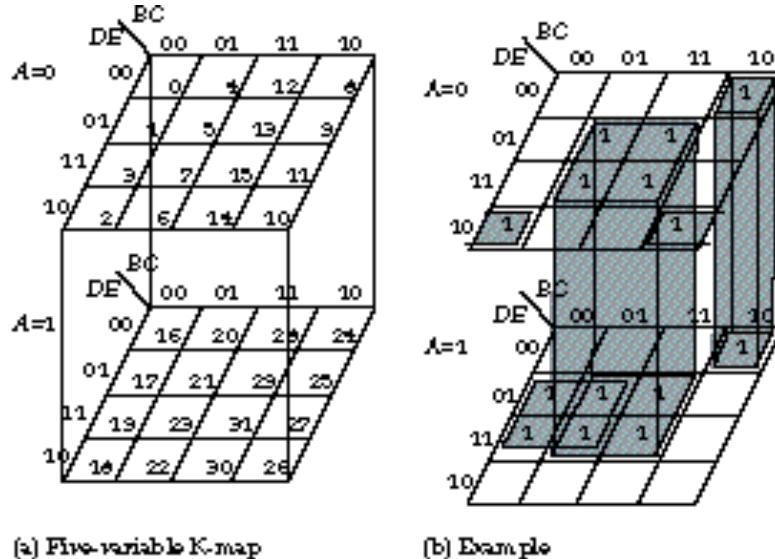

(a) Five-variable K-map

(b) Example

Figure 2.51 Five-variable K-map and example.

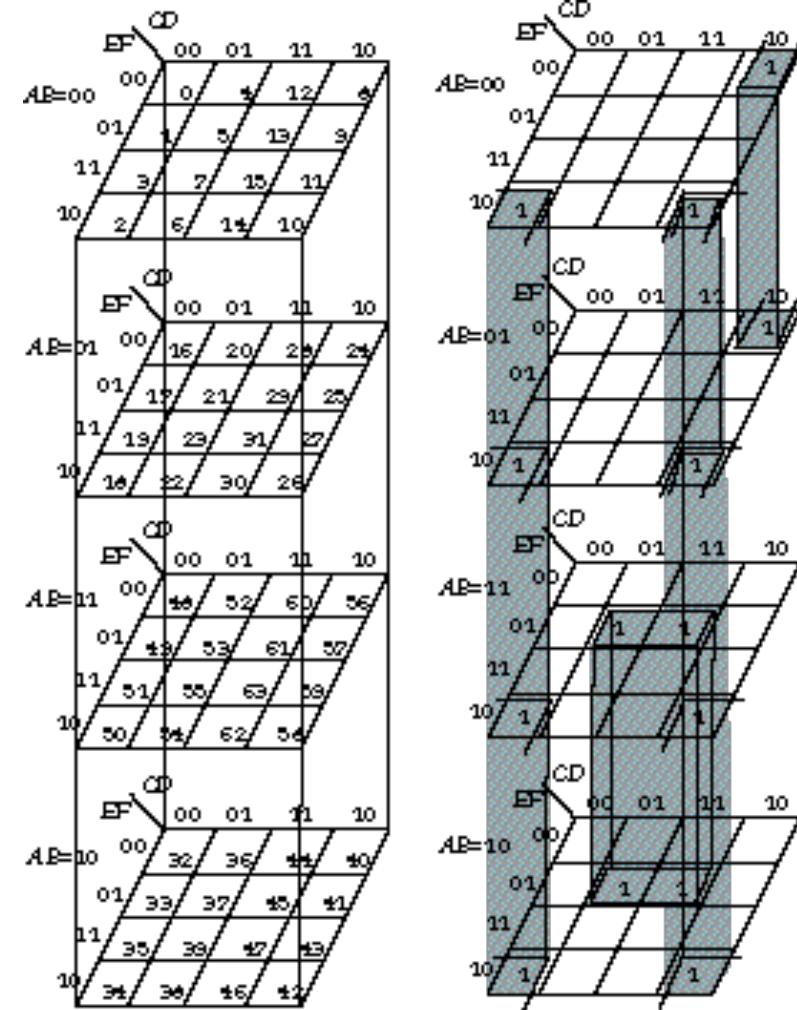

(a) Six-variable K-map

(b) Example

Figure 2.52 Six-variable K-map and example.